

Solutions for Chapter 2

Exercise 2.1

- a. Let h_0, h_1 be the switch logic for function x and g_0, g_1 the switch logic for function y . The index denotes, which logical value, 0 or 1, should be transferred. The Karnaugh–diagrams for both functions x and y describe the switch logic functions h_1 and g_1 , respectively.


		ab			
$x = h_1$		00	01	11	10
	0	0	0	1	0
	1	0	1	1	1

		ab			
$y = g_1$		00	01	11	10
	0	0	1	0	1
	1	1	0	1	0

$$h_1 = ab \vee ac \vee bc = ab \vee (a \vee b)c$$

$$g_1 = \bar{a}\bar{b}c \vee \bar{a}b\bar{c} \vee a\bar{b}\bar{c} \vee ab\bar{c} = (\bar{a}\bar{b} \vee ab)c \vee (\bar{a}b \vee a\bar{b})\bar{c}$$

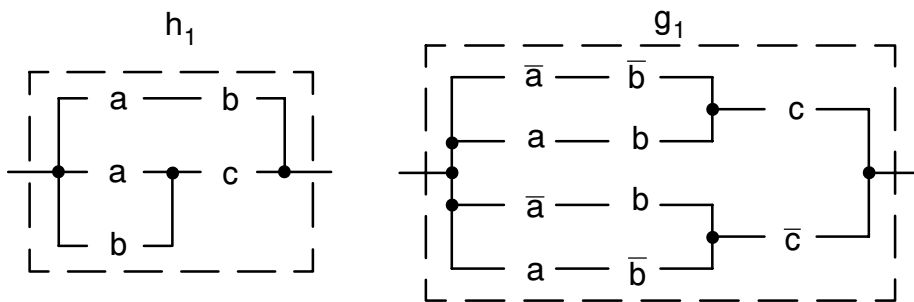The funktion h_1 comprises three blocks of two literals, whereas g_1 comprises four blocks of three literals. By factoring out the common variables c and \bar{c} the following switch functions can be derived:



The switch functions h_0 and g_0 , respectively, define the transfer of logical value 0, i.e., when the logical function equals 0 the switch function is 1.

		ab			
$\bar{x} = h_0$		00	01	11	10
	0	1	1	0	1
	1	1	0	0	0


		ab			
$\bar{y} = g_0$		00	01	11	10
	0	1	0	1	0
	1	0	1	0	1

Using the minterms for h_0 and g_0 , respectively, the following functions can be derived:

$$h_0 = \bar{a}\bar{b} \vee \bar{a}\bar{c} \vee \bar{b}\bar{c} = \bar{a}\bar{b} \vee (\bar{a} \vee \bar{b})\bar{c}$$


$$g_0 = \bar{a}\bar{b}\bar{c} \vee \bar{a}bc \vee ab\bar{c} \vee a\bar{b}c = (\bar{a}\bar{b} \vee ab)\bar{c} \vee (\bar{a}b \vee a\bar{b})c$$

leading to:

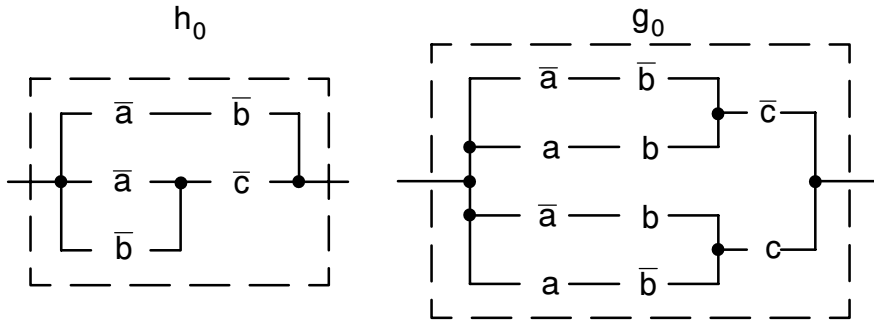

In this particular case the switch functions h_0 and g_0 have the same structure as h_1 and g_1 .

The overall function is given by:

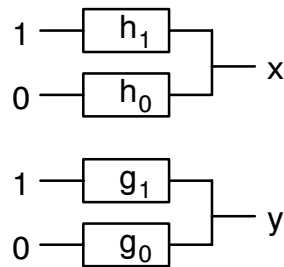

- b. The Karnaugh-diagram taken from a. can be transformed in a value entered diagram using c and \bar{c} as entered variables.

	ab			
x	00	01	11	10
	0	c	1	c


	ab			
y	00	01	11	10
	c	\bar{c}	c	\bar{c}

The functions above need switch logic functions h_0' , h_1' , h_c' , $h_{\bar{c}}'$ and g_0' , g_1' , g_c' , $g_{\bar{c}}'$, respectively.

Using the diagrams one obtains:

$$\begin{aligned} h_0' &= \bar{a}\bar{b} & g_c &= \bar{a}\bar{b} \vee ab \\ h_1' &= ab & g_{\bar{c}} &= \bar{a}b \vee a\bar{b} \\ h_c' &= \bar{a}b \vee a\bar{b} \end{aligned}$$

resulting in the switch logic functions:

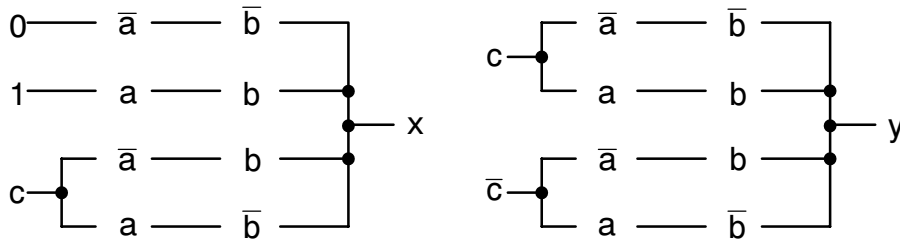

- c. The solution taken from part a. already represents a complex gate implementation. Only the switch functions for the transmission of value 1 and 0 have to be realized using p-channel and n-channel transistors, respectively. The p-channel transistors have to be controlled by complementary signals. Pseudo-NMOS can be implemented by h_0 and g_0 , respectively, and an additional pull-up transistor.
- d. Under the assumption that all the signals and their complements are available the transistor count is as follows:

n_{Tr}	x	y
Input signals 0,1	10	20
Input signals 0,1,c,c̄	8	8
Complex gates	10	20
Pseudo-NMOS	6	11

Exercise 2.2

a.

a	b	y
0	0	z
0	1	0
1	0	z
1	1	1

z means: path is in tristate mode, the level of output voltage is determined by the charging of the output capacitor.

Erroneous behaviour for $b = 0$.

b.

a	b	y
0	0	0
0	1	0
1	0	0
1	1	1

The logical function corresponds to the logical AND–function. The additional transistor guarantees a definite output level for $b=0$.

c. The two multiplexors mutually ensure a definite output level.

Exercise 2.3

a. T_1 saturation, because $u_{G1} = u_{D1} = U_{DD}$
 T_2 linear operation, because $u_X = u_{D2} < U_{DD} - U_T$

$$b. i_{DS1} = \frac{\beta}{2}(U_{DD} - u_X - U_T)^2$$

$$i_{DS2} = \beta \left[(U_{DD} - u_{out} - U_T)(u_X - u_{out}) - \frac{(u_X - u_{out})^2}{2} \right]$$

Solution: $i_{DS1} = i_{DS2}$ for $u_{out} = 0$

$$u_X = (U_{DD} - U_T)(1 - 1/\sqrt{2})$$

Condition for transistor switch off:

$$i_{DS1} = 0 \Rightarrow U_{DD} - u_X - U_T = 0$$

$$u_X = U_{DD} - U_T$$

$$i_{DS2} = 0 \Rightarrow u_X - u_{out} = 0$$

$$u_{out} = u_X$$

$$\text{and finally } u_{out} = U_{DD} - U_T$$

c. Using the solution from part b. we get:

$$u_{G3} = U_{DD} - U_T$$

$$u_{out} = u_{S3} = U_D - 2U_T$$

Conclusion: The output of a chain of pass–transistors should not be used to control other pass–transistors, because of the reduction of the voltage output level.

Exercise 2.4

a. $u_{DSn} = u_C$; $u_{GSn} = u_{in}$

Saturation: $u_C > (u_{in} - U_{Tn})/2$

$$u_{in} < 2u_C + U_{Tn}$$

$$i_{DS,Sat} = \beta/2 (u_{in} - U_{Tn})^2$$

b. Linear operation:

n : $U_{DSn} \leq (U_{GSn} - U_{Tn})/2$

p : $-U_{DSp} \leq (-U_{GSp} + U_{Tp})/2$


$$U_{DD} - u_C \leq (U_{DD} - u_{in} + U_{Tp})/2$$

$$u_{in} \leq 2u_C - U_{DD} + U_{Tp}$$

$$R_{Tn} = \frac{1}{\beta(U_{GSn} - U_{Tn})}$$

$$R_{Tp} = \frac{1}{\beta(-U_{GSp} + U_{Tp})} = \frac{1}{\beta(U_{DD} - u_{in} + U_{Tp})}$$

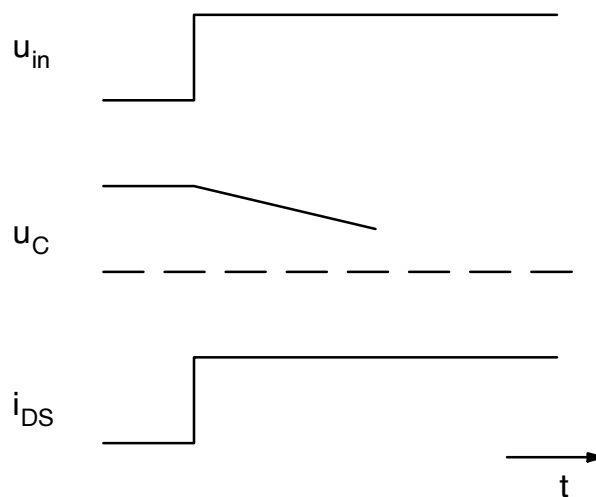c. Voltage and current waveforms over time



$$i_{DS,Sat} = \beta/2 (U_{DD} - U_T)^2 = 0,32 \beta U_{DD}^2$$

Discharging process with constant current


$$i_C(t) = C \frac{du_C}{dt} = -I_0 = \text{const}$$

$$u_C(t) = u_C(0) - \frac{1}{C} I_0 \cdot t$$

$$u_C(T) = U_{DD}/2 = U_{DD} - \frac{1}{C} I_0 T$$

$$T = \frac{U_{DD}}{2} \cdot \frac{C}{I_0} = \frac{U_{DD}}{2} \cdot \frac{C}{0,32 \beta U_{DD}^2} = \frac{C}{0,64 \beta U_{DD}}$$

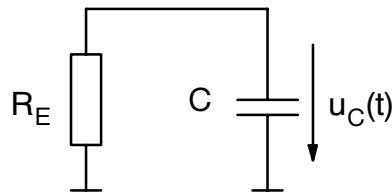d. Discharge process using an equivalent transistor resistance R_E :



$$u_C(t) = U_{DD} e^{-t/R_E C}$$

$$u_C(T) = U_{DD}/2 = U_{DD} e^{-T/R_E C}$$

$$T = \ln 2 R_E C$$

Transistor resistance


$$R_T(U_{GS} = U_{DD}) = \frac{1}{\beta(U_{DD} - U_T)} = \frac{1}{0,8 \beta U_{DD}}$$

Using the terms for T from part c. and d. leads to

$$T = \ln 2 R_E C = \frac{C}{0,64 \beta U_{DD}} = \frac{R_T C}{0,8}$$

$$R_E = \frac{1}{0,8 \ln 2} R_T \approx 1,80 R_T$$

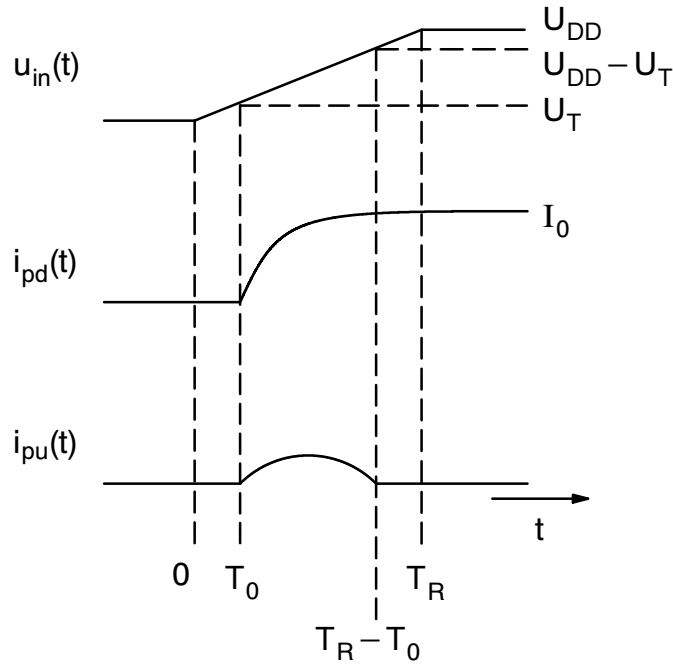e. Voltage and current waveforms over time



Simplification: $i_{pu}(t) = 0$

Time unit T_0 :

$$u_{in}(T_0) = U_T = 0,2U_{DD} = U_{DD} \frac{T_0}{T_R}$$

$$T_0 = \frac{U_T}{U_{DD}} T_R = 0,2T_R$$

Current: $i_{pd}(t)$ for $T_0 < t < T_R$

$$i_{pd}(t) = \frac{\beta}{2}(u_{in} - U_T)^2 = \frac{\beta}{2}\left(U_{DD} \frac{t}{T_R} - U_T\right)^2$$

$$= \frac{\beta}{2} U_{DD}^2 \left(\frac{t}{T_R} - \frac{U_T}{U_{DD}}\right)^2$$

$$= a \left(\frac{t}{T_R} - \frac{T_0}{T_R}\right)^2 = a(t' - 0,2)^2$$

$$a = \frac{\beta}{2} U_{DD}^2; \quad t' = \frac{t}{T_R} \text{ normalized time}$$

Saturation current for $t \geq T_R$:

$$i_{pd}(t) = I_0 = 0,64a$$

Discharging process:

$$i_{pd}(t) = -C \frac{du_C}{dt}$$

$$\int i_{pd}(t) dt = -C \int du_C$$

$$\int_{T_0}^{T_R} i_{pd}(t) dt + \int_{T_R}^T i_{pd}(t) dt = -C \int_{U_{DD}}^{U_{DD}/2} du_C$$

Normalization of time $t' = t/T_R$

$$T_R \int_{0,2}^1 i_{pd}(t') dt' + T_R \int_1^{T'} i_{pd}(t') dt' = CU_{DD}/2$$

$$\int_{0,2}^1 a(t' - 0,2)^2 dt' + \int_1^{T'} a \cdot 0,64 dt' = \frac{CU_{DD}}{2T_R}$$

$$a \frac{(t' - 0,2)^3}{3} \Big|_{0,2}^1 + a \cdot 0,64(T' - 1) = \frac{CU_{DD}}{2T_R}$$

$$a \frac{0,8^3}{3} + a \cdot 0,64T' - a \cdot 0,64 = \frac{CU_{DD}}{2T_R}$$

$$T' = 1 - \frac{0,8}{3} + \frac{CU_{DD}}{2T_R \cdot 0,64a} = 0,733 + \frac{T_C}{T_R}$$


Denormalization

$$T = 0,733 T_R + T_C$$

Time delay T_C at the input transition according to part c.


Exercise 2.5

a. $N=1$

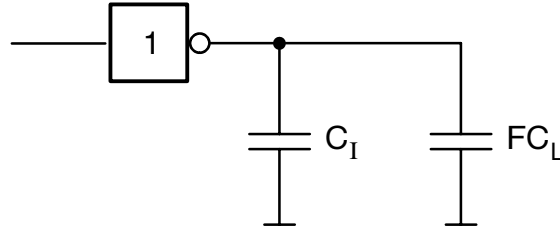

$$T_{D,1} = 2\tau_L + F\tau_L = (2 + F)\tau_L$$

b. Sketched for $N=3$

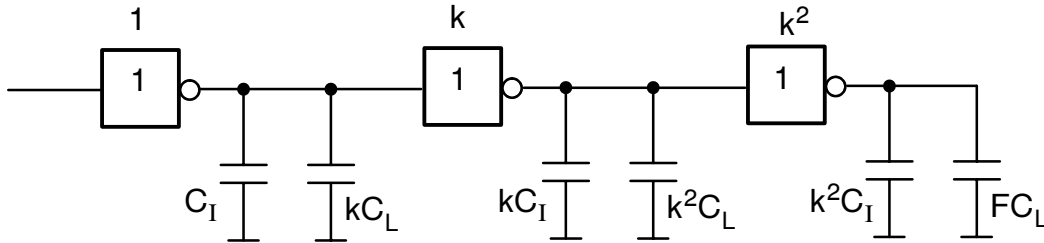

$$\begin{aligned} T_{D,N} &= (2\tau_L + k\tau_L) \\ &\quad + \frac{1}{k}(2k\tau_L + k^2\tau_L) \\ &\quad + \frac{1}{k^2}(2k^2\tau_L + k^3\tau_L) \\ &\quad + \dots \\ &\quad + \frac{1}{k^{N-1}}(2k^{N-1}\tau_L + F\tau_L) \\ &= (N-1)(2+k)\tau_L + 2\tau_L + \frac{F}{k^{N-1}}\tau_L \end{aligned}$$

$$\frac{\partial T_{D,N}}{\partial k} = (N-1)\tau_L - (N-1)\frac{F}{k^N}\tau_L \stackrel{!}{=} 0$$

$$k^N = F$$

$$k = F^{\frac{1}{N}}$$

$$T_{D,N,opt} = N(2 + F^{\frac{1}{N}})\tau_L$$

$$F = 1000$$

N	k	$T_{D,N}/\tau_L$	$A_{Si,N}/A_{Si,1}$	$T_{D,N} \cdot A_{Si,N}/\tau_L$
1	1000	1002	1	1002
2	31,6	67	33	2194
3	10,0	36	111	3996
4	5,62	30	216	6577
5	3,98	30	335	10024
6	3,16	31	463	14310
7	2,68	33	595	19480

The product $T_{D,N} \cdot A_{Si,N}$ increases with N , because the increase in the area needed is larger than the decrease of the time delay. For the product, the following expression holds approximately:

$$N \cdot F \left(1 + \frac{3}{k-1}\right) \tau_L$$

Exercise 2.6

- a. Let x_1, x_2 be equally distributed:
 $P(x_1=0) = P(x_1=1) = 0.5$; $P(x_2=0) = P(x_2=1) = 0.5$.
 NAND2: $P(y=1) = 0.75$

x_1	x_2	y
0	0	1
0	1	1
1	0	1
1	1	0

b.

				NAND2		NOR2	
$x_1(t)$	$x_1(t-1)$	$x_2(t)$	$x_2(t-1)$	$y(t)$	$y(t-1)$	$y(t)$	$y(t-1)$
0	0	0	0	1	1	1	1
0	0	0	1	1	1	1	0 (*)
0	0	1	0	1	1	0	1 (*)
0	0	1	1	1	1	0	0
0	1	0	0	1	1	1	0 (*)
0	1	0	1	1	0 (*)	1	0 (*)
0	1	1	0	1	1	0	0
0	1	1	1	1	0 (*)	0	0
1	0	0	0	1	1	0	1 (*)
1	0	0	1	1	1	0	0
1	0	1	0	0	1 (*)	0	1 (*)
1	0	1	1	0	1 (*)	0	0
1	1	0	0	1	1	0	0
1	1	0	1	1	0 (*)	0	0
1	1	1	0	0	1 (*)	0	0
1	1	1	1	0	0	0	0

Note: Changes of the output level have been marked by an asterisk.

c. According to the problem the variables x_1 and x_2 should be equally distributed, thus the transition activity function α is:

$$\alpha = \frac{6}{16}$$

d. $P(x_1) = P_1, P(x_2) = P_2$

$$\begin{aligned} \alpha(\gamma) = & (1 - \gamma) \cdot P_1 \cdot (1 - \gamma) \cdot P_2 + (1 - \gamma) \cdot P_1 \cdot \gamma \cdot P_2 + \\ & (1 - \gamma) \cdot P_1 \cdot \gamma \cdot P_2 + \gamma \cdot P_1 \cdot (1 - \gamma) \cdot P_2 + \\ & (1 - \gamma) \cdot P_1 \cdot (1 - \gamma) \cdot P_2 + \gamma \cdot P_1 \cdot (1 - \gamma) \cdot P_2 \end{aligned}$$

$$\begin{aligned} \alpha(\gamma) = & 2 \cdot ((1 - \gamma)^2 + 2 \cdot (1 - \gamma) \gamma) \cdot P_1 \cdot P_2 \\ = & 2 \cdot (1 - \gamma^2) \cdot P_1 \cdot P_2 \end{aligned}$$

using $P_1 = P_2 = 0.5$ and $\gamma = 0.75$, α can be calculated as

$$\alpha(0.75) = \frac{7}{32}.$$

- e. All results are the same (see function table in part b).
- f. The transition activity factor depends on the truth table of the logical function, the correlation between variables, and the transition probability for the variables.