

# Solutions for Chapter 3

## Exercise 3.1

a. Input  $b_i$  has to be complemented.


$a_n$	$b_n$	$c_n$	$\bar{b}_n$	$c_{n+1}$	$s$	
0	0	0	1	0	1	p
0	0	1	1	1	0	p
0	1	0	0	0	0	k
0	1	1	0	0	1	k
1	0	0	1	1	0	g
1	0	1	1	1	1	g
1	1	0	0	0	1	p
1	1	1	0	1	0	p

$$s_i = a_i \oplus \bar{b}_i \oplus c_i$$

$$c_{i+1} = a_i \bar{b}_i \vee a_i c_i \vee \bar{b}_i c_i$$

b. The Signals  $b_i$ ,  $c_i$  and  $c_{i+1}$  have negative weights.

$a_n$	$(b_n)$	$(c_n)$	$(c_{n+1})$	$s$	
0	0	0	0	0	p
0	0	1	1	1	p
0	1	0	1	1	g
0	1	1	1	0	g
1	0	0	0	1	k
1	0	1	0	0	k
1	1	0	0	0	p
1	1	1	1	1	p

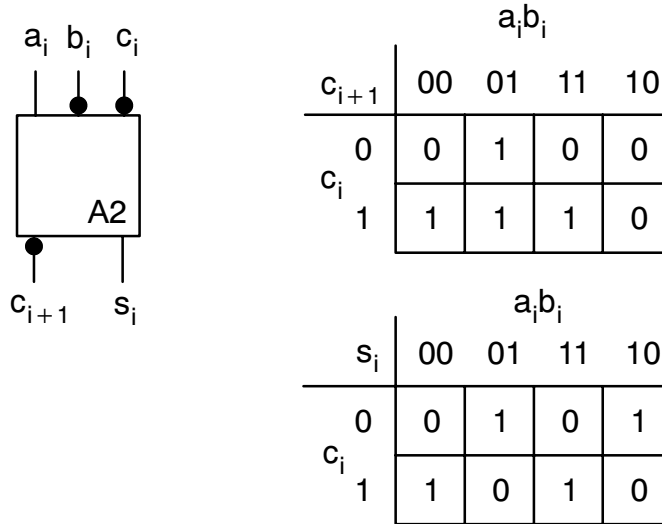

$$s_i = \bar{a}_i \bar{b}_i c_i \vee \bar{a}_i b_i \bar{c}_i \vee a_i \bar{b}_i \bar{c}_i \vee a_i b_i c_i$$

$$= a_i \oplus b_i \oplus c_i$$

$$c_{i+1} = \bar{a}_i b_i \vee \bar{a}_i c_i \vee b_i c_i$$

- c. Both implementations deliver the same bit pattern. The interpretation of the bit pattern, the numeric representation, depends on the numeric representation of the input operands.

If both input operands are positive dual numbers and the result has the same length  $n$  as the input operands, the result can be interpreted as a positive dual number as long as the first operand is always larger than or equal to the second operand. If in this case the first is at maximum by  $2^{n-1} - 1$  larger than the second operand or the second at maximum by  $2^{n-1}$  larger than the first, the result can be interpreted as a two's complement number.

In case of a wider result, yielded by a wider subtractor and extended input operands, the result can be interpreted as a two's complement number.

- d. a.:

$$g_i = a_i \bar{b}_i$$

$$p_i' = a_i \vee \bar{b}_i ; p_i = a_i \oplus \bar{b}_i$$

$$c_{i+1} = g_i \vee p_i c_i$$

$$s_i = p_i \oplus c_i$$

- b.:

$$g_i = \bar{a}_i b_i$$

$$p_i' = \bar{a}_i \vee b_i ; p_i = \bar{a}_i \oplus b_i$$

$$s_i = \bar{p}_i \oplus c_i$$

- e. Except for changed connections of the signalpairs  $b_i, \bar{b}_i, a_i, \bar{a}_i$  and  $p_i, \bar{p}_i$ , the structure of both implementations is identical. As a consequence, the transistor count and the circuit delay are the same.

### Exercise 3.2

- a. Delay NAND gate:

$$\text{NAND } m: T_{D,HL} = m(2+F)\tau_L$$

$$T_{D,LH} = (2+F)\tau_L$$

$$\text{INV} = \text{NAND } 1$$

$$\text{Assumption: } C_I = 2C_{L,0}$$

Carry path of a full adder

$$\begin{aligned} T_{D,VA,cc} &= T_{D,NAND2,LH} + T_{D,NAND3,HL} \\ &= (2+1)\tau_L + 3(2+F_c)\tau_L = (9+3F_c)\tau_L \end{aligned}$$

$$T_{0,cc} = 9\tau_L; \quad T_{1,cc} = 3\tau_L$$

Sum path of a full adder

$$\begin{aligned} T_{D,VA,cs} &= T_{D,INV} + T_{D,NAND3,LH} + T_{D,NAND4,HL} \\ &= (2+2)\tau_L + (2+1)\tau_L + 4(2+F_s)\tau_L \\ &= (15+4F_s)\tau_L \end{aligned}$$

$$T_{0,cs} = 15\tau_L; \quad T_{1,cs} = 4\tau_L$$


$T_0$  describes the load independent part of the delay.  $T_1$  describes the load dependent part, normalized to a fan-out factor of 1.

- b. Bit-Slice Adder

$$T_{D,ADD} = (n-1)T_{0,CC} + T_{0,cs}$$

$$T_{D,ADD} = (9n+6)\tau_L$$

Lookahead-Carry-Operator

 

$$\begin{aligned} (g_i, p_i) &= (g_j, p_j) \circ (g_k, p_k) \\ &= (g_j \vee p_j g_k, p_j p_k) \end{aligned}$$

$$T_{D,OP} = T_{0,OP} + T_{1,OP} F$$

$$= \begin{cases} (7 + 2F)\tau_L & HL \quad g_k \rightarrow g_i \\ (8 + F)\tau_L & LH \quad g_k \rightarrow g_i \end{cases}$$

Critical path of the carry block:

$$(g_0, P_0) \rightarrow (G_{n-2}, P_{n-2})$$

Number of operators in critical path:  $2 \log \frac{n}{2}$

$$\begin{aligned} T_{D, Carry-Block} &= 2 \log \frac{n}{2} T_{0, OP} \\ &= (2 \log n - 2) T_{0, OP} \end{aligned}$$

c. Bit-Slice Adder

Fan-in of one full adder input: 5

$$T_{D, ADD} = (n-1)F_c T_{1, cc} + T_{1, cs} F_s$$

$$F_c = 5 \text{ (Fan-Out Carry)}$$

$$T_{D, ADD} = (n-1) \cdot 15 \tau_L + 4 \tau_L F_s$$

Carry block of look-ahead carry adder:

Load of stage j:

$$\text{binary tree:} \quad 2 + j$$

$$\text{inverse binary tree;} \quad j$$

$$T_{D, Carry-Block} = \sum_{j=1}^{\log_2^n} [T_{1, OP} (2 + j) + T_{1, OP} j]$$

$$= 2T_{1, OP} \sum_{j=1}^{\log_2^n} (1 + j)$$

$$\sum_{j=1}^{\log_2^n} (1 + j) = \log \frac{n}{2} + \frac{1}{2} \log \frac{n}{2} (1 + \log \frac{n}{2})$$

$$= \frac{1}{2} \log^2 n + \frac{1}{2} \log n - 1$$

$$T_{D, Carry-Block} = (\log^2 n + \log n - 2) T_{1, OP}$$

- d. The delay characteristic of a circuit model may vary depending on the complexity of the model. In this example, the load neglecting model and the model

taking loads into account both show the same topology of the critical path. However, the consideration of the load leads to a totally different order of the delay characteristics for the binary look-ahead carry adder. Only as long as all outputs of all gates drive loads such that the delay of each gate is scaled by the same factor, the overall delay characteristics of both models can be safely assumed to be the same.

### Exercise 3.3

a. **Function  $F_\alpha$**

$$(GG_j, GP_j) = (g_{4j+3}, P_{4j+3}) \circ (g_{4j+2}, P_{4j+2}) \circ (g_{4j+1}, P_{4j+1}) \circ (g_{4j}, P_{4j})$$

$$GG_j = g_{4j+3} \vee P_{4j+3} g_{4j+2} \vee P_{4j+3} P_{4j+2} g_{4j+1} \vee P_{4j+3} P_{4j+2} P_{4j+1} g_{4j}$$

$$GP_j = P_{4j+3} P_{4j+2} P_{4j+1} P_{4j}$$

**Function  $F_\beta$**

$$(G_{4m+k}, P_{4m+k}) = (g_{4m+k}, P_{4m+k}) \circ (G_{4m+k-1}, P_{4m+k-1})$$

$$G_{4m} = g_{4m} \vee P_{4m} G_{4m-1}$$

$$P_{4m} = P_{4m} P_{4m-1}$$


$$G_{4m+1} = g_{4m+1} \vee P_{4m+1} g_{4m} \vee P_{4m+1} P_{4m} G_{4m-1}$$

$$P_{4m+1} = P_{4m+1} P_{4m} P_{4m-1}$$


$$G_{4m+2} = g_{4m+2} \vee P_{4m+2} g_{4m+1} \vee P_{4m+2} P_{4m+1} g_{4m} \\ \vee P_{4m+2} P_{4m+1} P_{4m} G_{4m-1}$$

$$P_{4m+2} = P_{4m+2} P_{4m+1} P_{4m} P_{4m-1}$$

 
b. 16 bit adder:  $F_{\alpha,16}, F_{\beta,16}$



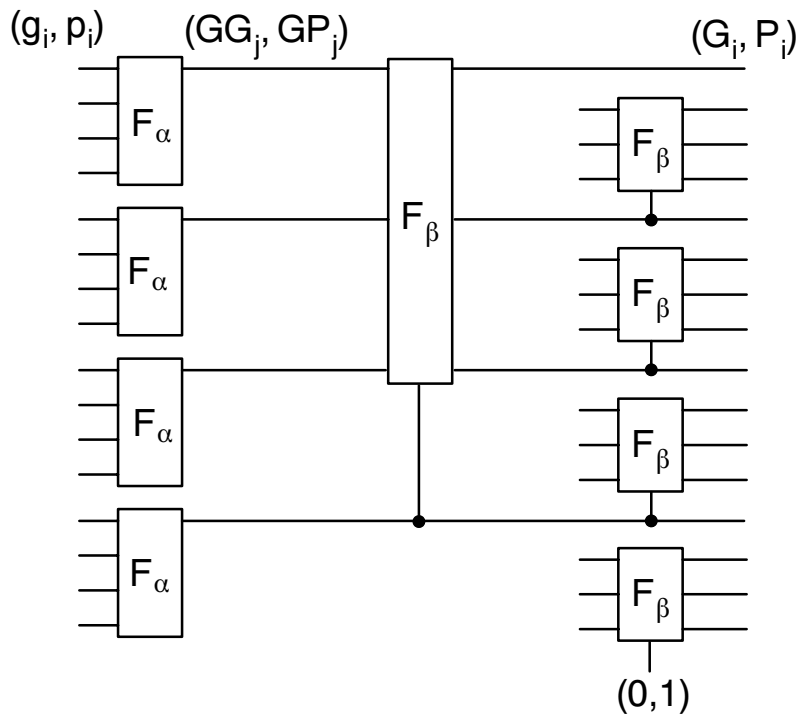
Alternative Solution (not considered in the following delay/transistor count calculations):



64 bit adder

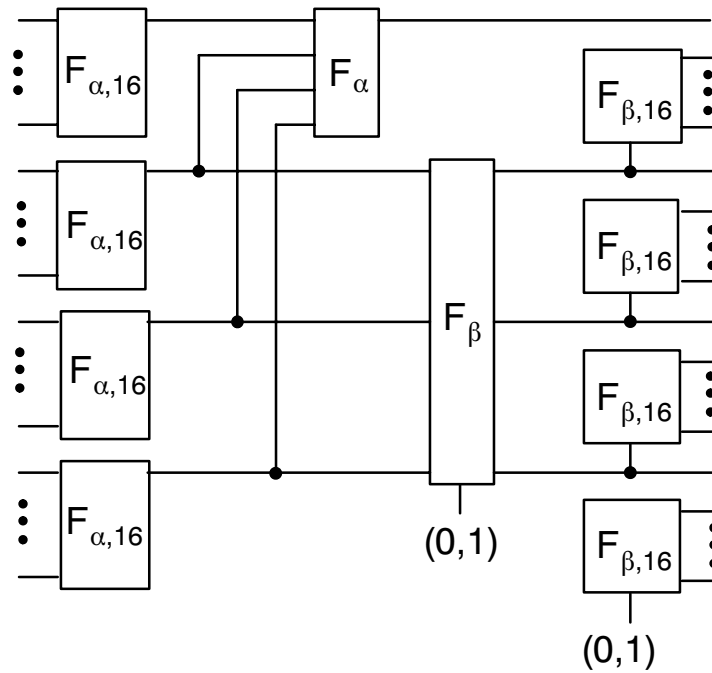

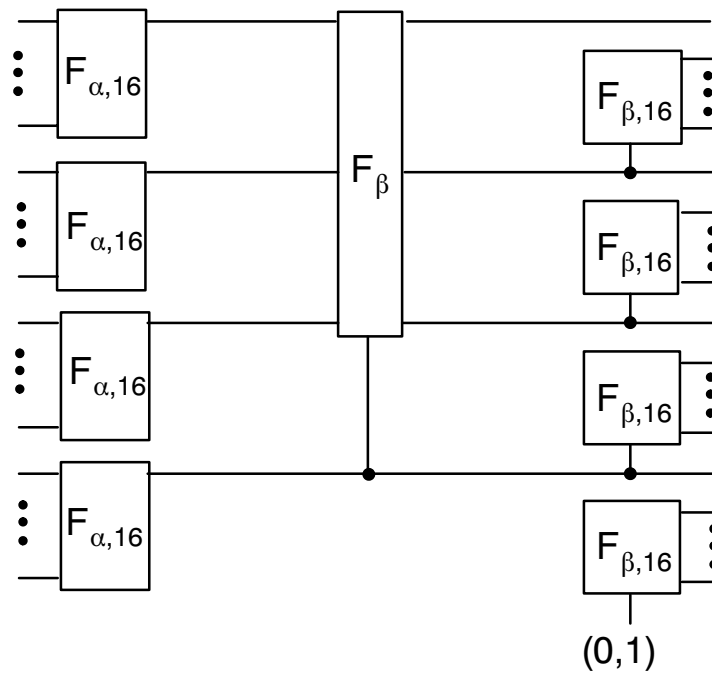Alternative Solution (not considered in the following delay/transistor count calculations):



- c. Binary–Lookahead–Carry:  $2 \log_2 n - 1$   
 Quartarnary – Lookahead–Carry:  $2 \log_4 n$
- d. Transistor count:  
 Binary–Lookahead–Carry:  
 Operator: 3 NAND2, 2 INV;  $n_{Tr} = 16$

$n$	$n_{OP}$	$N_{Tr}$
4	4	64
16	26	416
64	120	1920

Quartarnary–Lookahead–Carry:

$F_\alpha$ : 3 NAND4, NAND3, NAND2, 2INV;  $n_{Tr} = 38$

$F_\beta$ : 3 NAND4, 4NAND3, 5NAND2, 6INV;  $n_{Tr} = 80$

$n$	$n_\alpha$	$n_\beta$	$N_{Tr}$
4	1	1	118
16	5	5	590
64	21	21	2478

**Delay:**

Binary–Lookahead–Carry:

Operator:  $T_{D,OP} = (7 + 2F)\tau_L$

Critical Path

$n$	$n_{OP}$	Load $F$	$T_D/\tau_L$
4	2	3,1	22
16	6	3,4,5,3,2,1	78
64	10	3,...,7,5,...,1	150

Quartarnary–Lookahead–Carry:

$F_\alpha$ :  $T_{D,\alpha} = (11 + 4F)\tau_L$   $F_{in} = 1$

$F_\beta$ :  $T_{D,\beta} = (11 + 4F)\tau_L$   $F_{in} = 3$

Critical path


$n$	$n_\alpha$	Load $F$	$n_\beta$	Load $F$	$T_D/\tau_L$
4			1	1	15
16	1	4	2	4,1	69
64	2	4,4	3	7,4,1	135

Increased loads for  $(g_i, p_i)$  and differences between LH and HL transitions are not considered.



## Exercise 3.4


a.

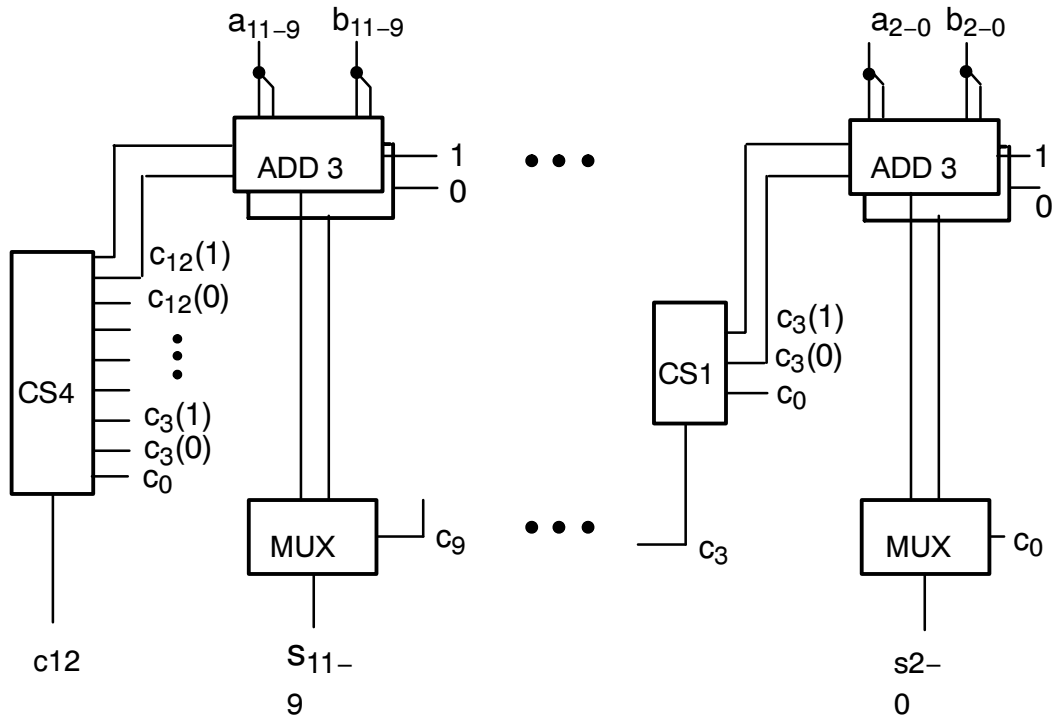

- b.
- CS1:  $c_3 = c_3(0) \vee c_3(1)c_0$
  - CS2:  $c_6 = c_6(0) \vee c_6(1)c_3(0) \vee c_6(1)c_3(1)c_0$
  - CS3:  $c_9 = c_9(0) \vee c_9(1)c_6(0) \vee c_9(1)c_6(1)c_3(0) \vee c_9(1)c_6(1)c_3(1)c_0$
  - CS4:  $c_{12} = c_{12}(0) \vee \dots \vee c_{12}(1)c_9(1)c_6(1)c_3(1)c_0$


### Exercise 3.5

a.

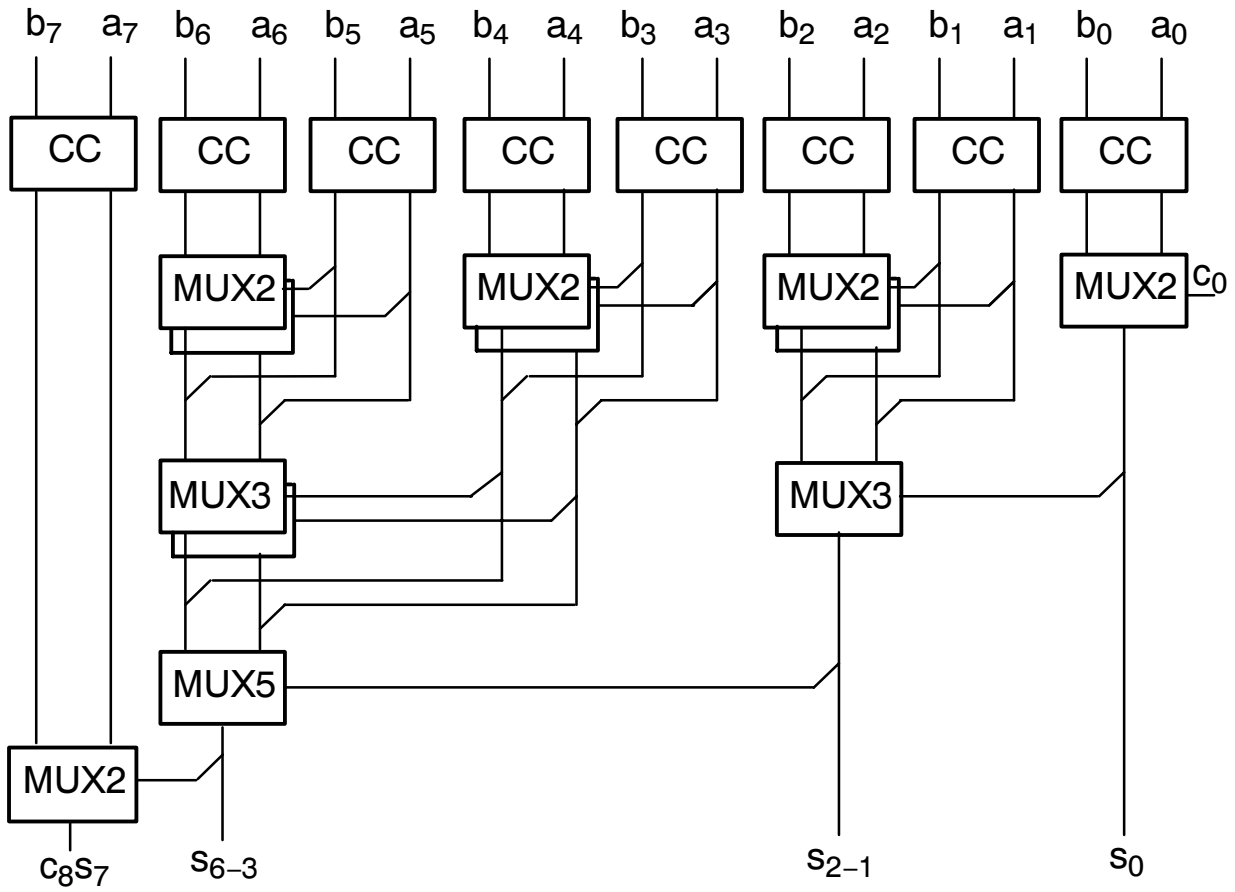


i		7	6	5	4	3	2	1	0
$a_i$		1	1	0	0	1	1	1	0
$b_i$		1	1	0	1	1	0	0	1
$s_i(0)$		0	0	0	1	0	1	1	1
$c_{i+1}(0)$		1	1	0	0	1	0	0	0
$s_i(1)$		1	1	1	0	1	0	0	
$c_{i+1}(1)$		1	1	0	1	1	1	1	
$s_i(0)$			0	0	0	0	1	1	1
$c_{i+1}(0)$			1		1		0		0
$s_i(1)$			0	1	0	1	0	0	
$c_{i+1}(1)$			1		1		1		
$s_i(0)$			0	1	0	0	1	1	1
$c_{i+1}(0)$			1				0		
$s_i(1)$			0	1	0	1			
$c_{i+1}(1)$			1						
$s_i(0)$		0	0	1	0	0	1	1	1
$c_{i+1}(0)$		1	1						
$s_i(1)$		1							
$c_{i+1}(1)$		1							
$s_i$		1	0	0	1	0	0	1	1

 - b. The result of the CC cell of the lowest significant bit slice can be used directly. In fact, a half adder can replace that cell.
- c. To break up transmission gate chains in multiplexer implementations, buffers should be used.



### Exercise 3.6

a.

 


Delay:

$$\begin{aligned}
 T_D &= T_{D,AND} + T_{D,FA,c',s} + T_{D,FA,c',c}(n - 3) + T_{D,FA,c',s} \\
 &+ T_{D,FA,s',s}(n - 3) + T_{D,FA,s',c} + T_{D,FA,c',c}(n - 2) + T_{D,FA,c',s} \\
 &= (4n - 5)T_0
 \end{aligned}$$

Operands for worst case delay:  
 (assuming inputs are initially zero)

$$A = 111111, B = 111111$$

b.

 

Delay:

$$T_D = T_{D,AND} + T_{D,FA,s',s}(n-2) + T_{D,FA,s',c} + T_{D,FA,c',c}(n-2) + T_{D,FA,c',s}$$

$$= (3n-2)T_0$$


Operands for worst case delay:

(assuming inputs are initially zero)


$$A = 111111, B = 111111$$

### Exercise 3.7

a.

 

b.

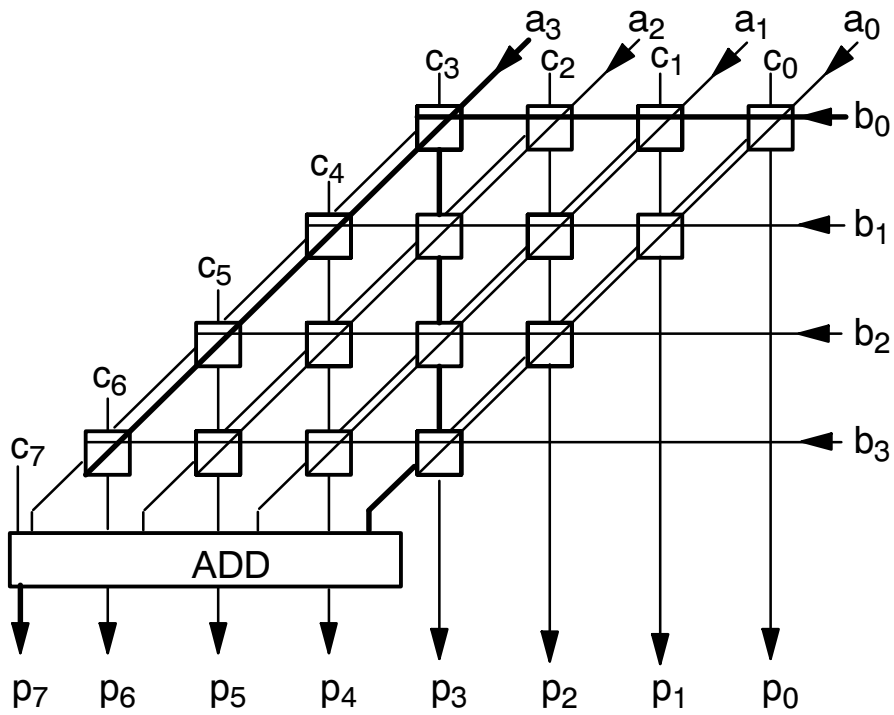

c.

Delay of the ripple carry multiplier/adder:

$$\begin{aligned}
 T_D &= T_{D,AND} + T_{D,FA,s',c} + 3T_{D,FA,c',c} + T_{D,FA,c',s} \\
 &+ 2T_{D,FA,s',s} + T_{D,FA,s',c} + 2T_{D,FA,c',c} + T_{D,FA,c',s} \\
 &= 7.5T_S
 \end{aligned}$$

Delay of the carry save multiplier/adder:

$$\begin{aligned}
 T_D &= T_{D,AND} + 3T_{D,FA,s',s} + T_{D,FA,s',c} + 3T_{D,FA,c',c} + T_{D,FA,c',s} \\
 &= 6T_S
 \end{aligned}$$

### Exercise 3.8

a.

4 bit counter;

$$s_0 = a \oplus b \oplus c \oplus d$$

$$s_1 = (a \vee b \vee c)(a \vee b \vee d)(a \vee c \vee d)(b \vee c \vee d)(\bar{a} \vee \bar{b} \vee \bar{c} \vee \bar{d})$$

$$s_2 = a b c d$$


5 bit counter:

$$s_0 = a \oplus b \oplus c \oplus d \oplus e$$

$$\begin{aligned}
 s_1 &= (a \vee b \vee c \vee d)(a \vee b \vee c \vee e)(a \vee b \vee d \vee e)(a \vee c \vee d \vee e) \\
 &(b \vee c \vee d \vee e)(\bar{a} \vee \bar{b} \vee \bar{c} \vee \bar{d})(\bar{a} \vee \bar{b} \vee \bar{c} \vee \bar{e}) \\
 &(\bar{a} \vee \bar{b} \vee \bar{d} \vee \bar{e})(\bar{a} \vee \bar{c} \vee \bar{d} \vee \bar{e})(\bar{b} \vee \bar{c} \vee \bar{d} \vee \bar{e})
 \end{aligned}$$

$$s_2 = a b c d \vee a b c e \vee a b d e \vee a c d e \vee b c d e \vee$$

b.

 


c.

$$k \geq \left\lceil \frac{\log n}{\log \frac{7}{3}} + 1 \right\rceil$$




## Exercise 3.9

a.

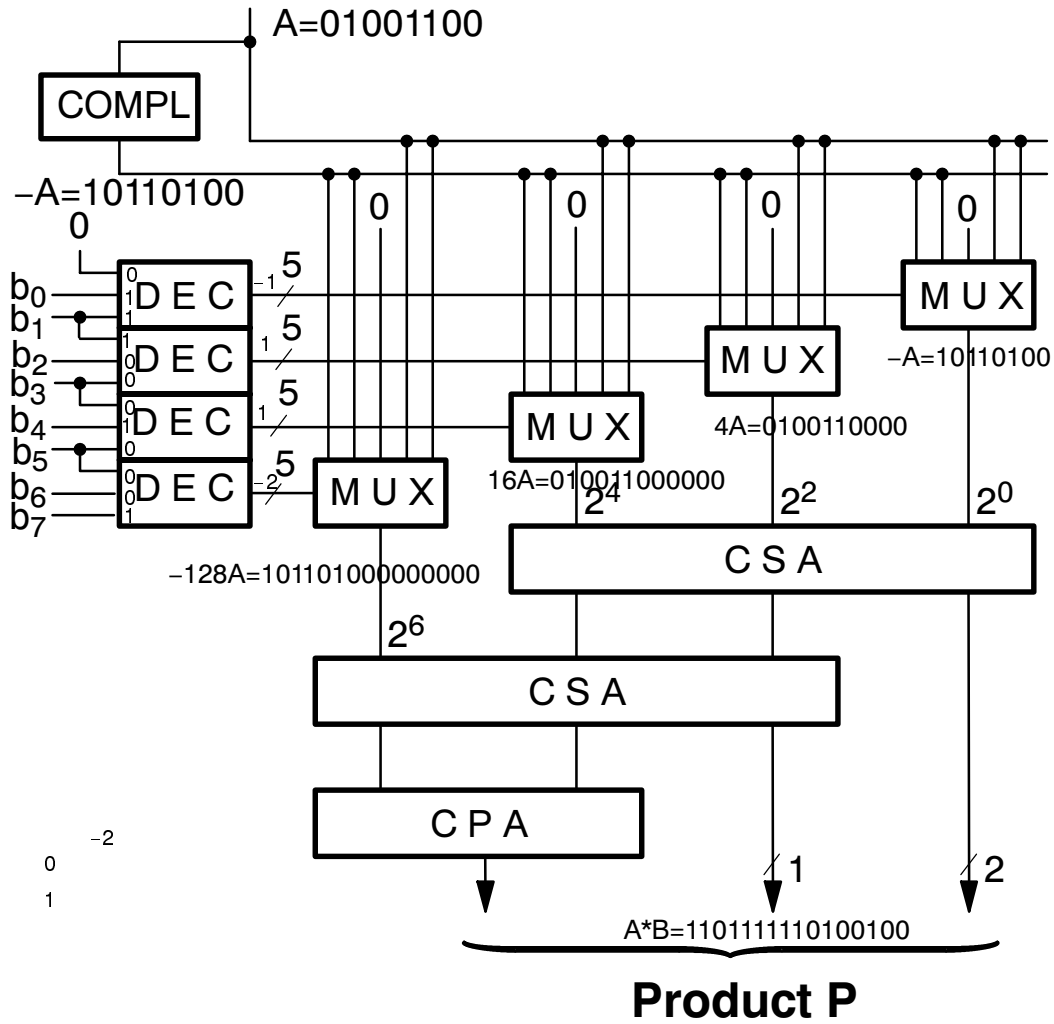


b.

 


### Exercise 3.10


a.

 


b.

 

c.

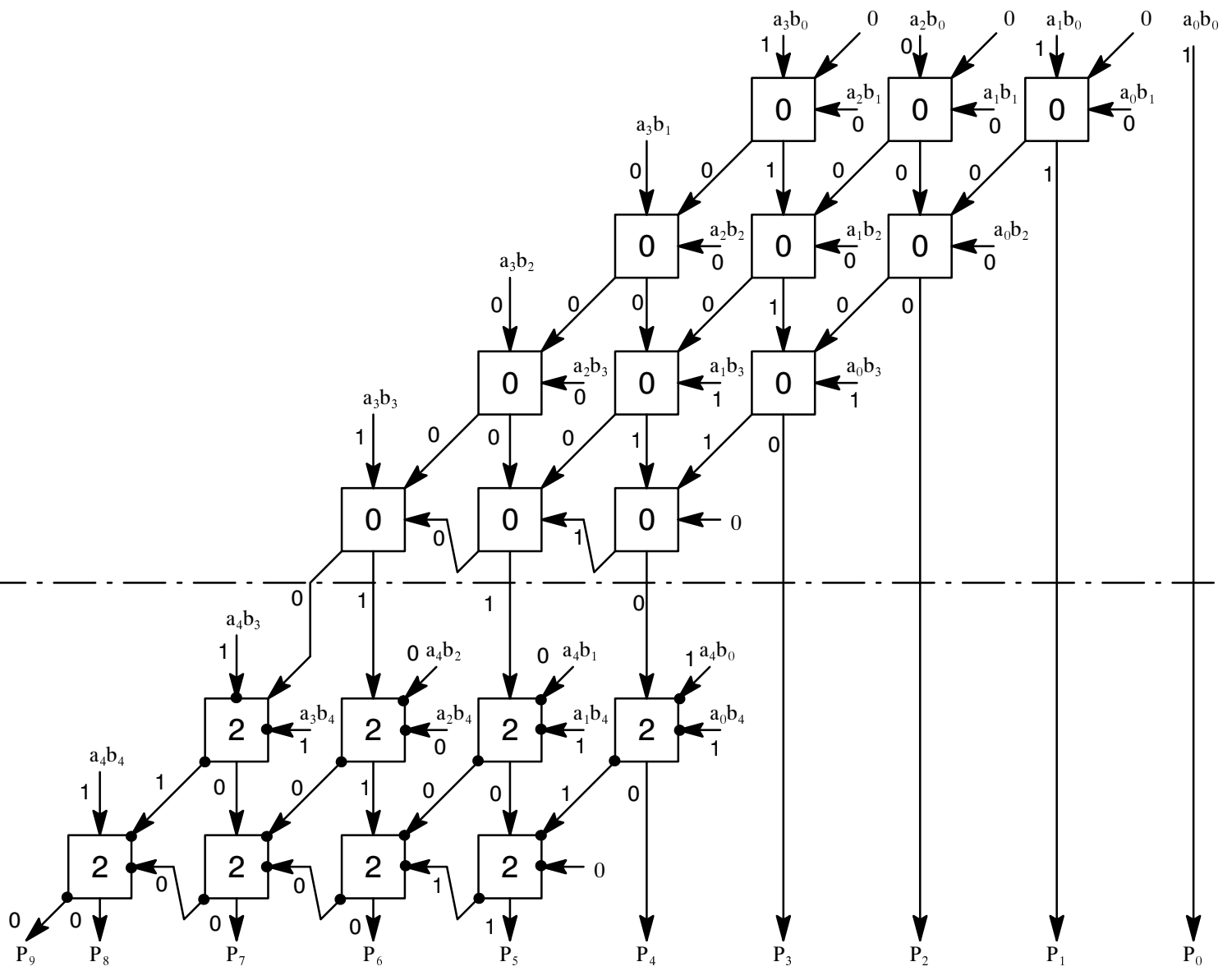



 

### Exercise 3.12

a. Correction factors  $k_m$ :

$m = 1$ : Sequence: 0,1,2,3,4,5  $k_m^{-1} = 1.6465$

$m = 0$ : Sequence: 1,2,3,4,5,6  $k_m^{-1} = 1$

$m = -1$ : Sequence: 1,2,3,4,4,5,6  $k_m^{-1} = 0.82330$

b. Calculation of  $\cos(z_0)$  and  $\sin(z_0)$

$x_0 = 1, y_0 = 0, z_0 = z_0, m = 1, z_n \rightarrow 0$

Result:

$x_6 = \cos(z_0) * k^{-1}$

$y_6 = \sin(z_0) * k^{-1}$

$i$	$x_i$	$y_i$	$z_i$	$\sigma_i$	$\text{atan}2^{-i}$	$k^{-i}$
0	1	0	0.10110	1	.11001	1.41
1	1	1	1.11101	-1	.01111	1.58
2	1.1	0.1	0.01100	1	.01000	1.64
3	1.011	0.111	0.00100	1	.00100	1.64
4	1.01000	1.00001	0.00000	1	.00010	1.65
5	1.00110	1.00011	1.11110	-1	.00001	1.65
Result	1.00111	1.00010	1.11111			

$\cos(z_0) = 1.00111_b / 1.65 = 0.76$

$\sin(z_0) = 1.00010_b / 1.65 = 0.64$

c. Multiplication by  $k$

$m = 0, y_0 = 0, x_0 = in, z = k, z_n \rightarrow 0, \text{Result: } y$

d.  $e^w : m = -1, x_0 = 1, y_0 = 1, z_0 = w, z_n \rightarrow 0, \text{Result: } x \text{ or } y$

$\sqrt{w} : m = -1, x_0 = w + .25, y_0 = w - .25, z_0 = 0, y_n \rightarrow 0, \text{Result: } x$